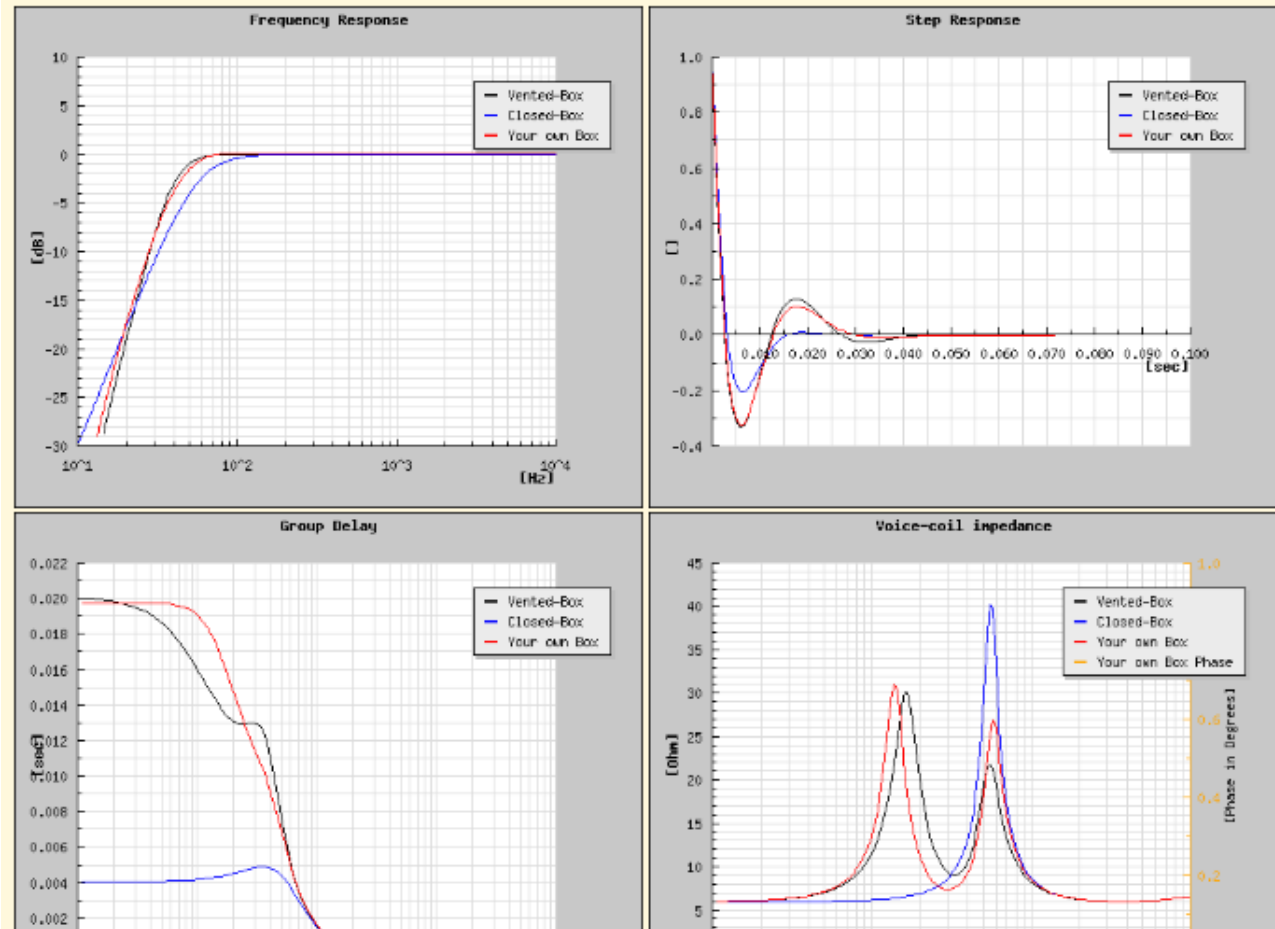




Result:	Vented-Box	Closed-Box without filling	Your own Box	Your own Box parameter for Spice Simulation
Volume of enclosure	56.09 litres	30.42 litres	40.00 litres	$f_s=26.00$ Hz $V_B=40.00$ litres
Resonance frequency	34.35 Hz	55.66 Hz	30.72 Hz	$V_{AS}=109.00$ litres $Q_L=4.50$
Half power frequency	39.91 Hz	55.71 Hz	42.65 Hz	$Q_{TS}=0.33$ $h=1.18$
Vent diameter	5 cm (19.63 cm <sup>2</sup> )	---	6 cm (28.27 cm <sup>2</sup> )	$Q_{MS}=2.23$
Vent length	5.20 cm	---	18.00 cm	$R_E=5.96$ Ohm
Reference efficiency	0.48 %	0.48 %	0.48 %	$L_E=0.53$ mH
Sound pressure level (SPL)	88.78 dB/W/m	88.78 dB/W/m	88.80 dB/W/m	$R_g=0.00$ Ohm



On top right you will find all parameters for a spice simulation.


Open your spice file with LTspice. Fill in parameter:

```
.param fs=26.0 Vas=109 Qts=0.33 Qms=2.23 Re=5.96 Le=0.53m Rg=1m
```

and


```
.param Vb=40.0 Ql=4.5 h=1.18
```

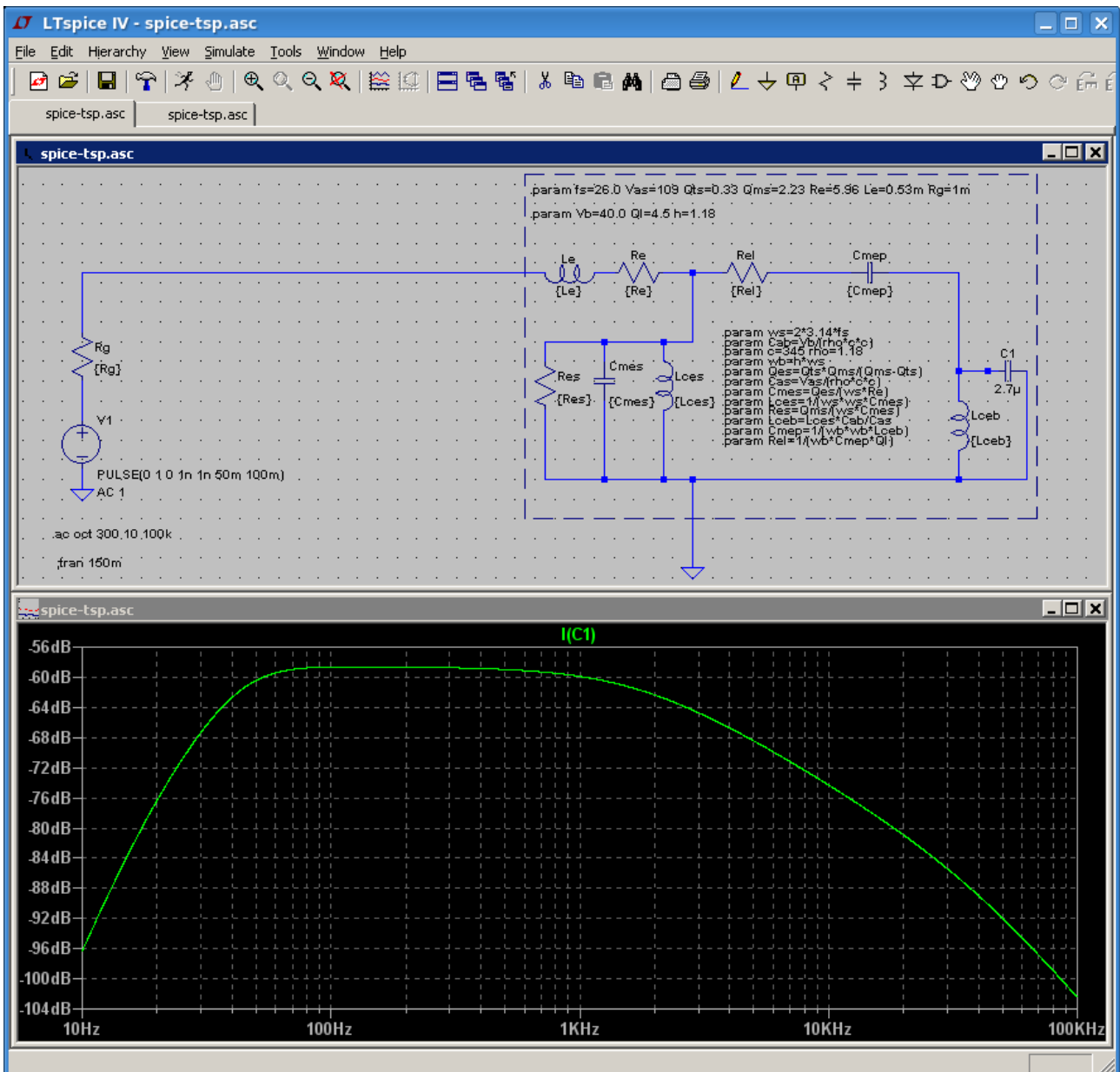To find the sound pressure frequency response start AC Analysis:




The current through the capacitor C1 corresponds to the sound pressure. The sound pressure fall-off (1kHz and higher) is caused by the voice coil inductance Le.

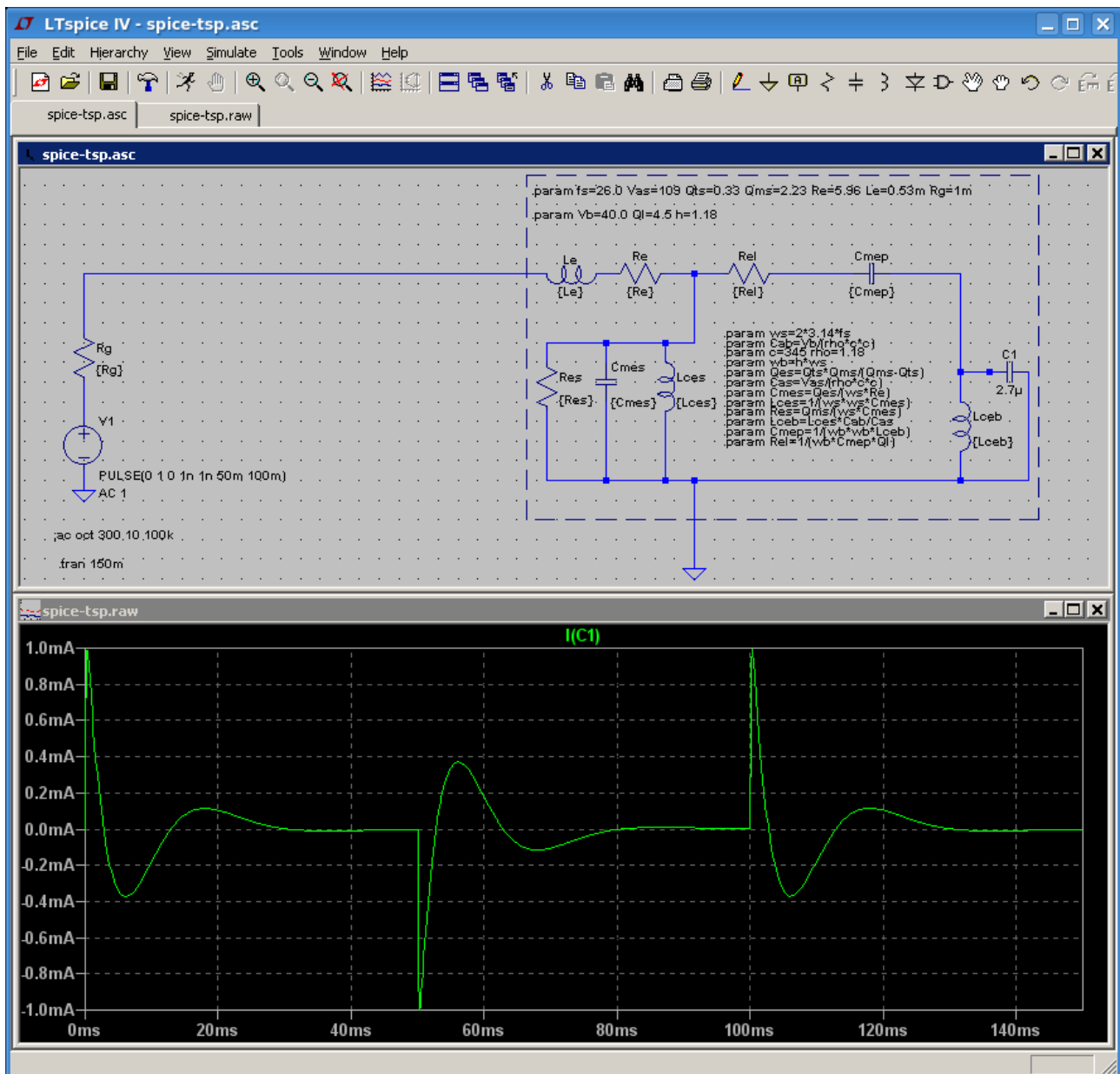To achieve a step response we must start a transient analysis:



You can vary the value of C1, but it should be small to minimize its influence on the circuit.

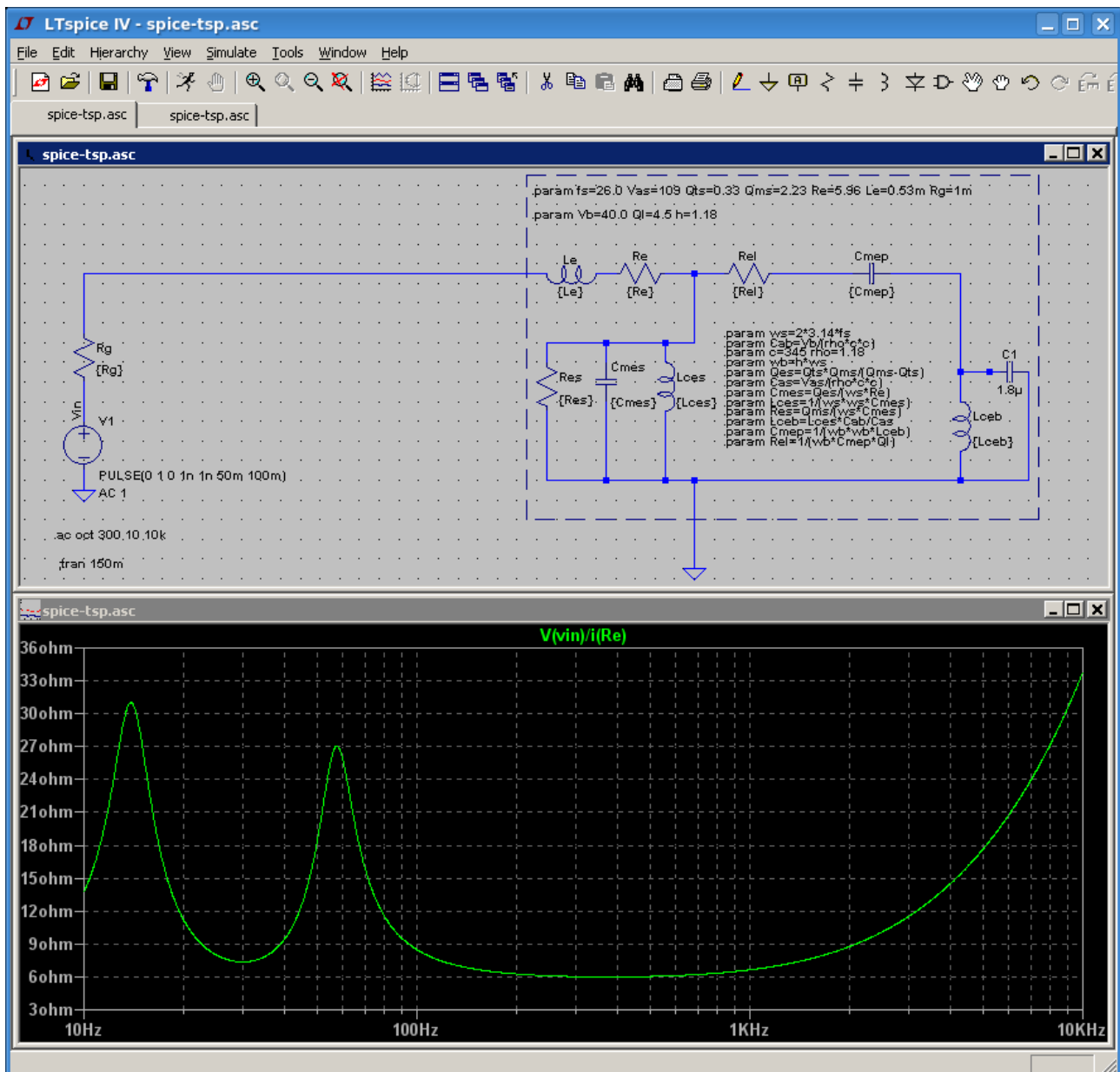Finally a simulation for a impedance response of the loudspeaker system:



Much fun!

Jürgen Micka [juergen@micka.de](mailto:juergen@micka.de)

© 2009

[www.micka.org](http://www.micka.org) or [www.micka.de/org](http://www.micka.de/org)